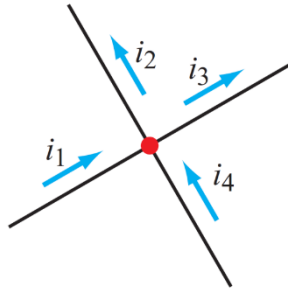


**KIRCHHOFF'S CURRENT LAW**, Sum of all currents entering a node is equal to zero

$$\sum_{n=1}^N i_n = 0 \quad (KCL)$$


$$i_1 + i_4 - i_2 - i_3 = 0$$



**KIRCHHOFF'S VOLTAGE LAW**

Sum of all voltage drops in a closed loop is equal to zero

$$\sum_{n=1}^N v_n = 0 \quad (KVL)$$

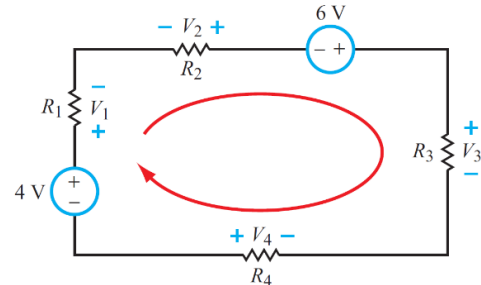


$$-4 + V_1 - V_2 - 6 + V_3 - V_4 = 0$$

**OHM'S LAW**  $V = iR$

**RESISTANCES IN PARALLEL:**  $\frac{1}{R_{eq}} = \sum_{i=1}^N \frac{1}{R_i}$  **RESISTANCES IN SERIES**  $R_{eq} = \sum_{i=1}^N R_i$

**THEVENIN'S EQUIVALENT CIRCUIT**

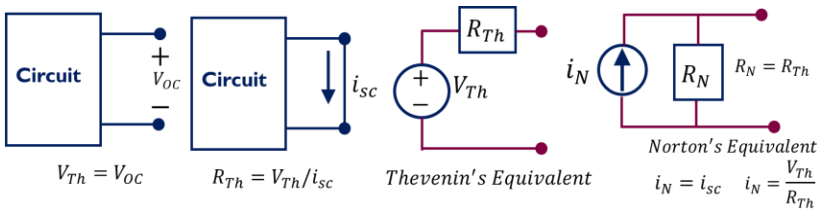

$V_{Th}$  = open circuit voltage

$R_{Th} = V_{th}/i_{sc}$

$R_{Th}$  is also the equivalent resistance seen between the terminals when all independent sources are set to zero

Norton's Equivalent circuit can be obtained from Thevenin's equivalent circuit using source transformation

**POWER ASSOCIATED WITH ANY CIRCUIT ELEMENT**


$$P = iV$$

**POWER DISSIPATED IN A RESISTOR**

$$P = iV = i^2 R = \frac{V^2}{R}$$

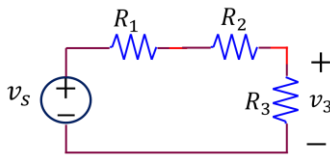**VOLTAGE DIVISION**


$$v_3 = v_s \frac{R_3}{R_1 + R_2 + R_3}$$



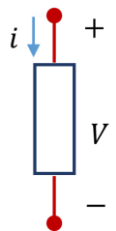
**PASSIVE POWER CONVENTION**

$$P = iV$$

positive  $P$  indicates absorbed power  
negative  $P$  indicates delivered power




**CURRENT DIVISION**

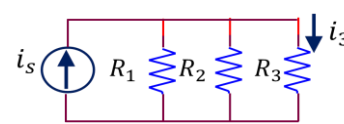

$$i_3 = i_s \frac{R_{eq}}{R_3}$$

$$R_{eq} = R_1 || R_2 || R_3$$

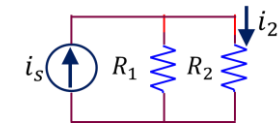


$$i_2 = i_s \frac{R_1}{R_1 + R_2}$$

**PRINCIPLE OF SUPERPOSITION:** For a linear system, the net response due to more than one input is the sum of the responses which would have been caused by each input individually.

Capacitor	Inductor
$i = C \frac{dv}{dt} \quad v = \frac{1}{C} \int_{t=t_0}^t i(t) dt + v(t_0)$ $P = iv \quad w = \frac{1}{2} C v^2$	$v = L \frac{di}{dt} \quad i = \frac{1}{L} \int_{t=t_0}^t v(t) dt + i(t_0)$ $P = iv \quad w = \frac{1}{2} L i^2$
Transient analysis for first order RC , general solution $v(t) = V_F + (V_0 - V_F) e^{-\frac{t}{\tau}} \quad t \geq 0$ $i(t) = I_0 e^{-\frac{t}{\tau}} \quad t \geq 0^+$	Transient analysis for first order RL circuits, general solution $v(t) = V_0 e^{-\frac{t}{\tau}} \quad t \geq 0^+$ $i(t) = I_F + (I_0 - I_F) e^{-\frac{t}{\tau}} \quad t \geq 0$
$\tau = RC$	$\tau = \frac{L}{R}$
$\Rightarrow v(0^-) = v(0) = v(0^+) = V_0$	$i(0^-) = i(0) = i(0^+) = I_0$
<b>Sinusoidal steady state analysis</b>	
$\tilde{V} = Z \tilde{I} \quad Z = \frac{1}{j\omega C}$	$\tilde{V} = Z \tilde{I} \quad Z = j\omega L$
$v(t) = V_m \cos(\omega t), \quad i(t) = I_m \cos(\omega t + 90^\circ)$ Current leads voltage by $90^\circ$	$i(t) = I_m \cos(\omega t) \quad v(t) = V_m \cos(\omega t + 90^\circ)$ Current lags voltage by $90^\circ$
Capacitors in parallel $C_{eq} = \Sigma C_i$	Inductors in parallel $\frac{1}{L_{eq}} = \Sigma \frac{1}{L_i}$
Capacitor in series $\frac{1}{C_{eq}} = \Sigma \frac{1}{C_i}$	Inductors in series $L_{eq} = \Sigma L_i$

$$v(t) = V_m \cos(\omega t + \theta_v) \xleftrightarrow{\text{Phasor transform}} \tilde{V} = V_m \angle \theta_v = V_m e^{j\theta_v}$$

#### SOURCE TRANSFORMATION

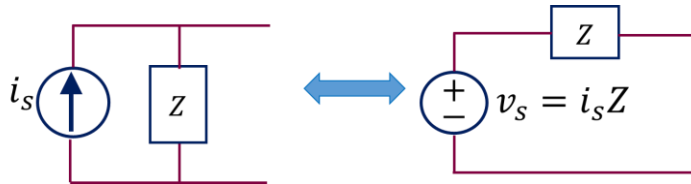

#### SAMPLING AND QUANTIZATION

Sampling rate  $f_s \geq 2f_{max}$  , minimum sampling rate is called the Nyquist rate

$N$  = number of bits,  $L$  = number of quantization Levels

$\Delta$  = quantization step,  $q_e$  = quantization error

$V_{FS}$  = full scale range of the analog to digital converter, A/D

For a digital system of  $N$  bits, the number of discrete levels  $L = 2^N$

Quantization step  $\Delta = \frac{V_{FS}}{L} = \frac{V_{FS}}{2^N}$

$V_{FS}$  is the full scale range of A/D  $V_{FS} = V_{max} - V_{min}$

$V_{max}$  is the maximum allowed input level for A/D

$V_{min}$  is the minimum allowed input level for A/D

Quantization error  $q_e \leq \frac{\Delta}{2}$  if signal is within A/D range

If the signal exceeds the A/D full scale range, the error will be given by




$$q_e = V_{signal} - \left( V_{max} - \frac{\Delta}{2} \right) \quad \text{for } V_{signal} > V_{max}$$

$$q_e = \left( V_{min} + \frac{\Delta}{2} \right) - V_{signal} \quad \text{for } V_{signal} < V_{min}$$

For an A/D that has an allowed input range of *from*  $-10V$  to  $10V$ , then  $V_{FS} = 10 - (-10) = 20V$
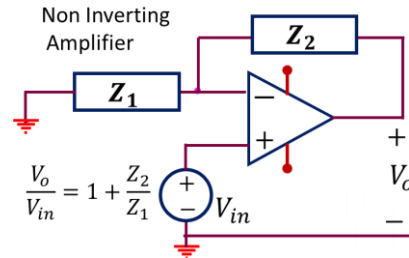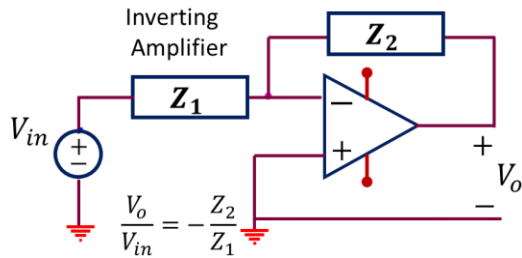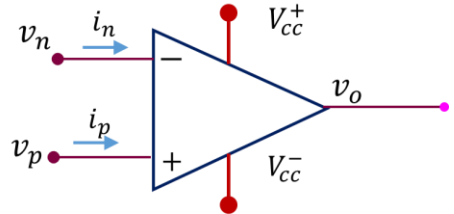
### IDEAL OPERATIONAL AMPLIFIER

- $i_n = 0, i_p = 0 \quad v_n = v_p$
- Infinite resistance looking into the inverting or non-inverting terminal
- Infinite bandwidth
- For linear mode of operation  $V_{cc}^- \leq v_o \leq V_{cc}^+$



### TRANSFER FUNCTIONS AND THE FREQUENCY RESPONSE OF LINEAR SYSTEMS

$$H(j\omega) = \frac{v_o}{v_{in}}$$

$$v_{in}(t) = A \cos(\omega_0 t) \xrightarrow{H(j\omega)} v_o(t) = A |H(j\omega_0)| \cos(\omega_0 t + \phi)$$

$$H(j\omega_0) = |H(j\omega_0)| \angle \phi(\omega_0)$$