

# EECE 2150: Quiz 1 Notesheet - Sean Balbale - September 18, 2024

## 1. Basic Circuit Elements

### 1.1 Resistors

A **resistor** resists the flow of electric charge. The resistance  $R$  is a function of size, shape, and material:

$$R = \frac{\rho \ell}{A} = \frac{\ell}{\sigma A}$$

where:

- $\rho$  is the resistivity,
- $\sigma$  is the conductivity,
- $\ell$  is the length,
- $A$  is the cross-sectional area.

**Ohm's Law:** Voltage  $V$ , current  $I$ , and resistance  $R$ :

$$V = IR \quad \text{or} \quad I = \frac{V}{R}$$

*Example:* A resistor of  $10\ \Omega$  has  $5\text{ V}$  applied across it. The current is:


$$I = \frac{5\text{ V}}{10\ \Omega} = 0.5\text{ A}$$

**Power Dissipation:** The power dissipated by a resistor:

$$P = IV = I^2 R = \frac{V^2}{R}$$

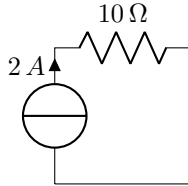*Example:* If  $2\text{ A}$  flows through a  $10\ \Omega$  resistor, the power dissipated is:

$$P = I^2 R = (2\text{ A})^2 \times 10\ \Omega = 40\text{ W}$$



### 1.2 Conductance

Conductance  $G$  is the reciprocal of resistance:

$$G = \frac{1}{R} \quad (\text{Siemens, } S = \Omega^{-1})$$

### 1.3 Ideal Conductors

An **ideal conductor** has infinite conductivity  $\sigma \rightarrow \infty$ , and zero resistance  $R = 0$ .

## 2. Circuit Laws

### 2.1 Kirchhoff's Current Law (KCL)

The sum of all currents entering a node equals the sum of all currents leaving the node:

$$\sum_{k=1}^n i_k = 0$$

*Example:* If three currents enter a node ( $2\text{ A}$ ,  $4\text{ A}$ ,  $3\text{ A}$ ) and one current exits ( $i_x$ ):

$$2\text{ A} + 4\text{ A} + 3\text{ A} = i_x$$

$$i_x = 9\text{ A}$$

### 2.2 Kirchhoff's Voltage Law (KVL)

The sum of all voltage drops in a closed loop equals the sum of all voltage rises:

$$\sum_{k=1}^n v_k = 0$$

*Example:* In a loop with three voltage drops ( $10\text{ V}$ ,  $8\text{ V}$ ,  $4\text{ V}$ ) and an applied voltage of  $24\text{ V}$ :


$$10\text{ V} + 8\text{ V} + 4\text{ V} + V_x = 24\text{ V}$$

$$V_x = 2\text{ V}$$

## 3. Types of Sources

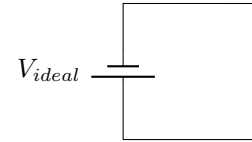
### 3.1 Ideal Voltage and Current Sources

An **ideal voltage source** maintains a constant voltage regardless of the current. An **ideal current source** maintains a constant current regardless of the voltage across it.


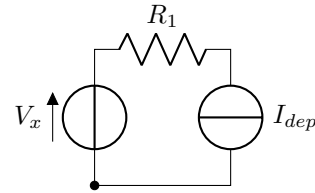
### 3.2 Dependent Sources

A **dependent source** provides a voltage or current depending on the voltage or current elsewhere in the circuit.



## 4. Voltage, Current, Power, and Polarity

### 4.1 Voltage

Voltage  $V$  is the electric potential difference between two points in a circuit:

$$v = \frac{dw}{dq}$$

where  $v$  is voltage,  $w$  is energy, and  $q$  is charge.

## 4.2 Current

**Direct Current (DC):** A constant current over time.

**Alternating Current (AC):** A sinusoidal current, e.g., 60 Hz.

## 4.3 Power

Power is the rate of expending or absorbing energy:

$$P = VI$$


**Polarity Reference:** - If current enters the positive terminal, the element absorbs power:

$$P = VI$$

- If current enters the negative terminal, the element delivers power:

$$P = -VI$$

## 4.4 Polarity Reference Diagrams

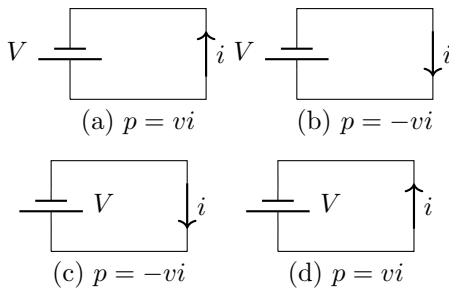


## 5. Practice Problems

### Problem 1: Ohm's Law

A  $15\Omega$  resistor has a current of  $2A$ . What is the voltage across the resistor?

**Solution:**

$$V = IR = 2A \times 15\Omega = 30V$$

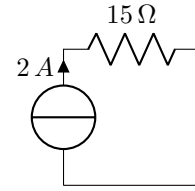


### Problem 2: Power Dissipation

A  $50\Omega$  resistor has  $10V$  across it. Find the power dissipated.

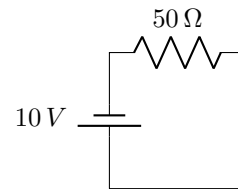**Solution:**

$$P = \frac{V^2}{R} = \frac{10^2}{50} = 2W$$



### Problem 3: Kirchhoff's Current Law

At a node, currents of  $3A$ ,  $4A$ , and  $2A$  enter, and a current of  $5A$  leaves. Find the unknown current  $i_x$ .

**Solution:**

$$3A + 4A + 2A = 5A + i_x$$

$$i_x = 4A$$