

## 1. Basic Circuit Elements

### 1.1 Resistors

**Resistor** resists the flow of charge. The resistance  $R$  is a function of length, area, and resistivity:

$$R = \frac{\rho \ell}{A} \quad \text{or} \quad R = \frac{\ell}{\sigma A}$$

- $\rho$ : Resistivity
- $\ell$ : Length
- $A$ : Area

**Ohm's Law:** Voltage, current, and resistance are related:

$$V = IR \quad \text{or} \quad I = \frac{V}{R}$$

*Example:* If  $V = 10\text{ V}$  and  $R = 5\ \Omega$ , then  $I = \frac{10\text{ V}}{5\ \Omega} = 2\text{ A}$ .

**Power Dissipation:**

$$P = IV = I^2 R = \frac{V^2}{R}$$

### 1.2 Conductance

Conductance is the reciprocal of resistance:

$$G = \frac{1}{R} \quad \text{in Siemens (S)}$$

### 1.3 Ideal Conductors

$$R = 0, \quad \sigma \rightarrow \infty$$

No voltage drop across an ideal conductor.

## 2. Circuit Laws

### 2.1 Kirchhoff's Current Law (KCL)

The sum of currents entering a node equals the sum of currents leaving the node:

$$\sum_{k=1}^n i_k = 0$$

*Example:* At a node,  $2\text{ A}$ ,  $3\text{ A}$ , and  $5\text{ A}$  enter. If  $i_x$  leaves, then:

$$2 + 3 + 5 = i_x \quad \Rightarrow \quad i_x = 10\text{ A}$$

### 2.2 Kirchhoff's Voltage Law (KVL)

The sum of voltage drops in a loop equals the sum of voltage rises:

$$\sum_{k=1}^n v_k = 0$$

*Example:* In a loop with three voltage drops  $10\text{ V}$ ,  $6\text{ V}$ , and  $4\text{ V}$  and a supply voltage  $V_s = 24\text{ V}$ :

$$10 + 6 + 4 + V_x = 24 \quad \Rightarrow \quad V_x = 4\text{ V}$$

## 3. Resistors in Series and Parallel

### 3.1 Series Resistors

Resistors in series share the same current:

$$R_{\text{eq}} = R_1 + R_2 + \cdots + R_n$$

**Voltage Division:** The voltage across  $R_k$  is:

$$V_k = V_s \frac{R_k}{R_{\text{eq}}}$$

*Example:* For two resistors in series,  $R_1 = 10\ \Omega$  and  $R_2 = 5\ \Omega$ , and the source voltage  $V_s = 30\text{ V}$ :

$$V_1 = 30 \frac{10}{15} = 20\text{ V}, \quad V_2 = 30 \frac{5}{15} = 10\text{ V}$$

### 3.2 Parallel Resistors

Resistors in parallel share the same voltage:

$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2} + \cdots + \frac{1}{R_n}$$

**Current Division:**

$$i_k = I_s \frac{R_{\text{eq}}}{R_k}$$

*Example:* For two resistors in parallel,  $R_1 = 6\ \Omega$  and  $R_2 = 3\ \Omega$ , and a total current  $I_s = 6\text{ A}$ :

$$\frac{1}{R_{\text{eq}}} = \frac{1}{6} + \frac{1}{3} = \frac{1}{2} \quad \Rightarrow \quad R_{\text{eq}} = 2\ \Omega$$

$$i_1 = 6\text{ A} \times \frac{2}{6} = 2\text{ A}, \quad i_2 = 6\text{ A} \times \frac{2}{3} = 4\text{ A}$$

### 3.3 Series-Parallel Combination Example

Find the equivalent resistance of the following circuit:

$R_1 = 4\ \Omega$ ,  $R_2 = 6\ \Omega$  (in parallel),  $R_3 = 2\ \Omega$  (in series)

$$\frac{1}{R_{\text{eq1}}} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{4} + \frac{1}{6} = \frac{5}{12} \quad \Rightarrow \quad R_{\text{eq1}} = 2.4\ \Omega$$

$$R_{\text{total}} = R_{\text{eq1}} + R_3 = 2.4\ \Omega + 2\ \Omega = 4.4\ \Omega$$

## 4. Sources

### 4.1 Independent Sources

**Ideal Voltage Source:** Constant voltage irrespective of current.


**Ideal Current Source:** Constant current irrespective of voltage.

## 4.2 Dependent Sources

**Dependent Voltage Source:** Voltage depends on a current or voltage elsewhere.

**Dependent Current Source:** Current depends on a current or voltage elsewhere.

## 4.3 Example

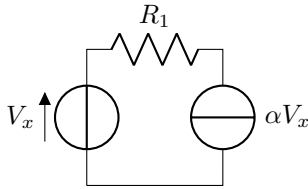

## 5. Equivalent Resistance and $\Delta$ -Y Conversion

### 5.1 Simplification of Resistive Networks

To simplify circuits:

- Combine series and parallel resistors.
- Reduce complex networks step-by-step.

### 5.2 Delta-Wye ( $\Delta$ -Y) Conversion

For resistors in a delta configuration, the equivalent Y-resistance is calculated as:

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}, \quad R_2 = \frac{R_a R_c}{R_a + R_b + R_c}, \quad R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

**Example:** For a delta network with  $R_a = 10 \Omega$ ,  $R_b = 20 \Omega$ , and  $R_c = 30 \Omega$ :

$$R_1 = \frac{20 \times 30}{10 + 20 + 30} = 12 \Omega, \quad R_2 = \frac{10 \times 30}{60} = 5 \Omega, \quad R_3 = \frac{10 \times 20}{60} = 3.33 \Omega$$

## 6. Passive Sign Convention

In the passive sign convention:

- If current enters through the positive terminal of an element, the element is absorbing power:

$$P = VI$$

- If current enters through the negative terminal, the element is delivering power:

$$P = -VI$$

### 6.1 Example: Power Calculation

*Example:* A  $12 V$  source supplies a current of  $2 A$  to a resistor. Power delivered by the source:

$$P = -VI = -(12 V)(2 A) = -24 W$$

This means the source is delivering  $24 W$  of power.

## 7. Practice Problems

### Problem 1: Ohm's Law

A  $10 \Omega$  resistor has a current of  $1.5 A$ . What is the voltage across it?

**Solution:**

$$V = IR = 1.5 A \times 10 \Omega = 15 V$$

### Problem 2: Equivalent Resistance

Find the equivalent resistance of  $4 \Omega$  and  $6 \Omega$  in parallel.

**Solution:**

$$\frac{1}{R_{eq}} = \frac{1}{4} + \frac{1}{6} = \frac{5}{12} \Rightarrow R_{eq} = 2.4 \Omega$$